



Matrusri Engineering College

Sponsored by Matrusri Education Society, Estd.:1980
An Autonomous Institution | Approved by AICTE, Affiliated to Osmania University
#16-1-486, Saidabad, Hyderabad-500059, Ph:040-24072764
Department of Computer Science and Engineering



Assignment II

Class/Branch: III SEM CSE B & D

Date: 17.10.2025

Subject: Digital Logic Design

Max Marks: 10

Syllabus: Unit II

Minimization Techniques: The minimization with theorems, The Karnaugh Map Method, Three, Four and Five variable K- Maps, Quine-McCluskey Method

Combinational Circuits: Full adder, Subtractor, Multiplexer, Demultiplexer, Encoder, Decoder, Gray to Binary and Binary to Gray converter

COURSE OUTCOMES (COs):

After the completion of the course students will be able to	
CO1	Understand the design process of digital hardware, use Boolean algebra to minimize the logical expressions and optimize the implementation of logical functions.
CO2	Understand the number representation and design combinational circuits like adders, MUX etc.
CO3	Design Combinational circuits using programmable logic devices.
CO4	Analyse sequential circuits using flip-flops and design the registers & counters.
CO5	Represent a sequential circuit using Finite State machine and apply state minimization techniques to design a FSM

Q.No	Question	CO	BL
PART-A		Short Answer Question	
1.	Compare a) encoder and decoder with neat diagrams. b) multiplexer and demultiplexer with neat diagrams.	CO2	L2
2.	Design full adder and full subtractor circuits.	CO2	L2
PART-B		Long Answer Question	
3.	Simplify the following expressions using K-Map and realize the logic circuit. (a) $F = \pi M(1, 2, 3, 8, 9, 10, 11, 14)$. $\pi d(7, 15)$ (b) $F = \sum m(0, 2, 5, 9, 15) + \sum d(6, 7, 8, 10, 12, 13)$ (c) $F = b' + ac' + a'cd$	CO2	L4
4.	Minimize the following function using tabular method and realize with universal gates. (a) $F = \sum m(0, 2, 5, 9, 15) + \sum d(6, 7, 8, 10, 12, 13)$ (b) $F(w, x, y, z) = \sum m(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$	CO2	L2
5.	Design a 4 bit Gray to Binary code converter with circuit diagram.	CO2	L3

